

گزارش کار تمرین کامپیوتری سری اول

محمد مبین جلودار – 402101493

Q1)

- $Z_{RL} = 20 + j10 \Omega,$
- $Z_C = -jX_C = -j\frac{1}{2\pi fC}.$

The imaginary part of $\frac{1}{Z_{total}}$ is:

$$\text{Imaginary part} = \text{Imaginary part of } \frac{1}{Z_{RL}} + \text{Imaginary part of } \frac{1}{Z_C}$$

$$\frac{1}{Z_{RL}} = \frac{1}{20 + j10} \times \frac{20 - j10}{20 - j10} = \frac{20 - j10}{(20)^2 + (10)^2}$$

$$\frac{1}{Z_{RL}} = \frac{20 - j10}{500} = 0.04 - j0.02$$

$$\text{Imaginary part of } \frac{1}{Z_{RL}} + \text{Imaginary part of } \frac{1}{Z_C} = 0$$

$$-0.02 + (2\pi fC) = 0$$

$$2\pi fC = 0.02$$

$$C = \frac{0.02}{2\pi f}$$

$$C = \frac{0.02}{2\pi(50)} = \frac{0.02}{314.16} \approx 0.0000637 \text{ F}$$

$$C \approx 63.7 \mu\text{F}$$

Since the capacitors are arranged in a triangle, this value must be multiplied by three:

$$C_{\text{final}} = 3 \times 63.7 \mu\text{F}$$

$$C_{\text{final}} = 191.1 \mu\text{F}$$


The values of the various elements are as follows:

R1=1,R2=20

L1=0.03/P H,L2=0.02/P H,L3=0.03/P H,L4=0.1/P H


C(In the star arrangement)=200/P uF

N2:N1 = 2rad3

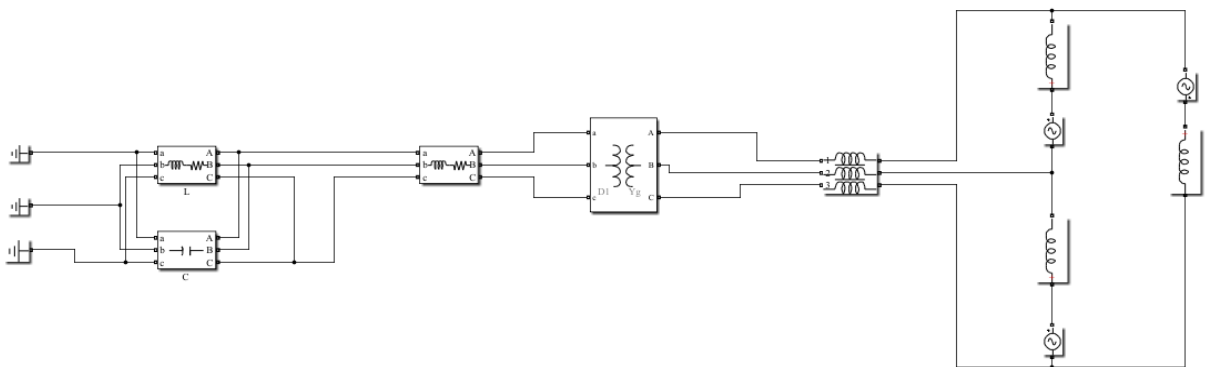

We implemented the circuit as above.

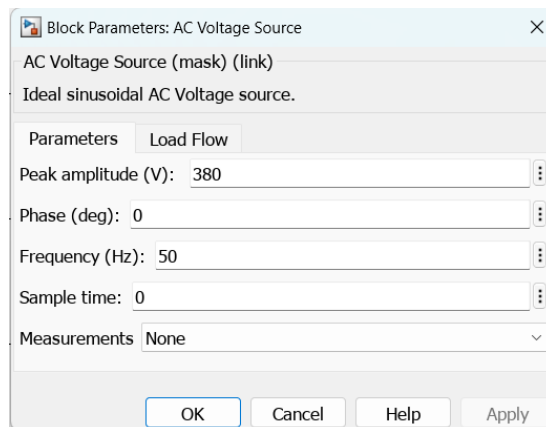The data sheets of the various elements are as follows:



Block Parameters: AC Voltage Source

AC Voltage Source (mask) (link)

Ideal sinusoidal AC Voltage source.

Parameters Load Flow

Peak amplitude (V): 380

Phase (deg): 0


Frequency (Hz): 50

Sample time: 0

Measurements None

OK Cancel Help Apply

AC voltage source inside the generator

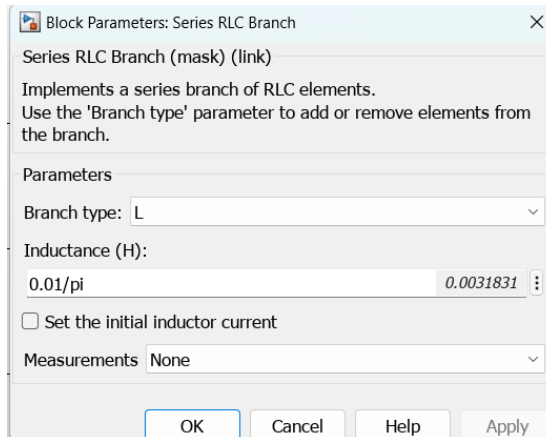

Block Parameters: Series RLC Branch

Series RLC Branch (mask) (link)

Implements a series branch of RLC elements.
Use the 'Branch type' parameter to add or remove elements from the branch.

Parameters

Branch type: L

Inductance (H): 0.01/pi 0.0031831

☐ Set the initial inductor current

Measurements None

OK Cancel Help Apply

Inductor inside the generator

Block Parameters: Mutual Inductance

Mutual Inductance (mask) (link)

Implements inductances with mutual coupling.

Parameters

Type of mutual inductance: Two or three windings with equal mutual terms

Winding 1 self impedance [R1(Ohm) L1(H)]:
[1e-03 0.02/pi] [0.001,0.0063662]

Winding 2 self impedance [R2(Ohm) L2(H)]:
[1e-03 0.02/pi] [0.001,0.0063662]

☒ Three windings Mutual Inductance

Winding 3 self impedance [R3(Ohm) L3(H)]:
[1e-03 0.02/pi] [0.001,0.0063662]

Mutual impedance [Rm(Ohm) Lm(H)]:
[0 0.01/pi] [0,0.0031831]

Measurements None

OK Cancel Help Apply

Transmission line coupling inductors

Block Parameters: Three-Phase Transformer (Two Windings)

Three-Phase Transformer (Two Windings) (mask) (link)

This block implements a three-phase transformer by using three single-phase transformers. Set the winding connection to 'Yn' when you want to access the neutral point of the Wye.

Click the Apply or the OK button after a change to the Units popup to confirm the conversion of parameters.

Configuration Parameters

Winding 1 connection (ABC terminals): Yg

Winding 2 connection (abc terminals): Delta (D1)

Core

Type: Three single-phase transformers

☐ Simulate saturation

Measurements None

OK Cancel Help Apply

Block Parameters: Three-Phase Transformer (Two Windings)

Three-Phase Transformer (Two Windings) (mask) (link)

This block implements a three-phase transformer by using three single-phase transformers. Set the winding connection to 'Yn' when you want to access the neutral point of the Wye.

Click the Apply or the OK button after a change to the Units popup to confirm the conversion of parameters.

Configuration Parameters

Units SI

Nominal power and frequency [Pn(VA) , fn(Hz)] [250e6 , 60] [250000000,60]

Winding 1 parameters [V1 Ph-Ph(Vrms) , R1(Ohm) , L1(H)] [380 1e-3 1e-3]

Winding 2 parameters [V2 Ph-Ph(Vrms) , R2(Ohm) , L2(H)] [760 1e-3 1e-3]

Magnetization resistance Rm (Ohm) 1e3

Magnetization inductance Lm (H) 1e3

Saturation characteristic [i1(A) , phi1(V.s) ; i2 , phi2 ; ...] 1910.3;277.72 2419.7

OK Cancel Help Apply

Three-phase transformer

Block Parameters: Series RLC Branch3

Series RLC Branch (mask) (link)

Implements a series branch of RLC elements.
Use the 'Branch type' parameter to add or remove elements from the branch.

Parameters

Branch type: RL

Resistance (Ohms):
1

Inductance (H):
0.03/pi 0.0095493

☐ Set the initial inductor current

Measurements: None

OK Cancel Help Apply

Resistance and inductance in transmission lines

Block Parameters: Series RLC Branch6

Series RLC Branch (mask) (link)

Implements a series branch of RLC elements.
Use the 'Branch type' parameter to add or remove elements from the branch.

Parameters

Branch type: RL

Resistance (Ohms):
20

Inductance (H):
0.1/pi 0.031831


☐ Set the initial inductor current

Measurements: None

OK Cancel Help Apply

Resistance and inductance in load

Two wattmeter method:

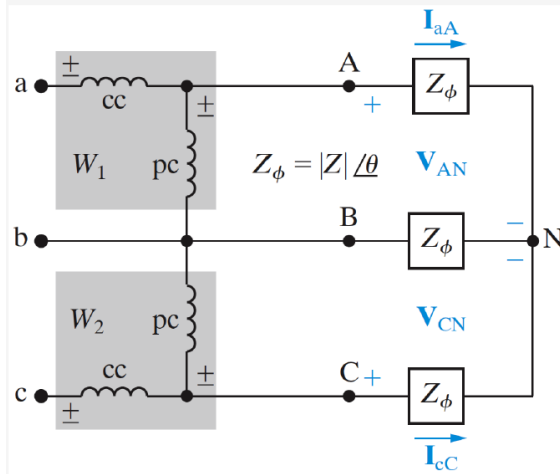


• روش دو واتمتری (هر نوع بار متعادل یا نامتعادل ستاره یا مثلث)


$$\begin{aligned}
 W_1 &= v_{AB} i_{aA} = (v_{AN} - v_{BN}) i_{aA} \\
 W_2 &= v_{CB} i_{cC} = (v_{CN} - v_{BN}) i_{cC} \\
 W_1 + W_2 &= v_{AN} i_{aA} + v_{BN} (-i_{aA} - i_{cC}) + v_{CN} i_{cC} \\
 i_{aA} + i_{bB} + i_{cC} &= 0 \Rightarrow i_{bB} = -i_{aA} - i_{cC} \\
 W_1 + W_2 &= v_{AN} i_{aA} + v_{BN} i_{bB} + v_{CN} i_{cC} = W
 \end{aligned}$$

• در اثبات این رابطه از متعادل بودن بار استفاده نشده است!

• برای بار مثلث دلخواه هم این رابطه قابل اثبات است.

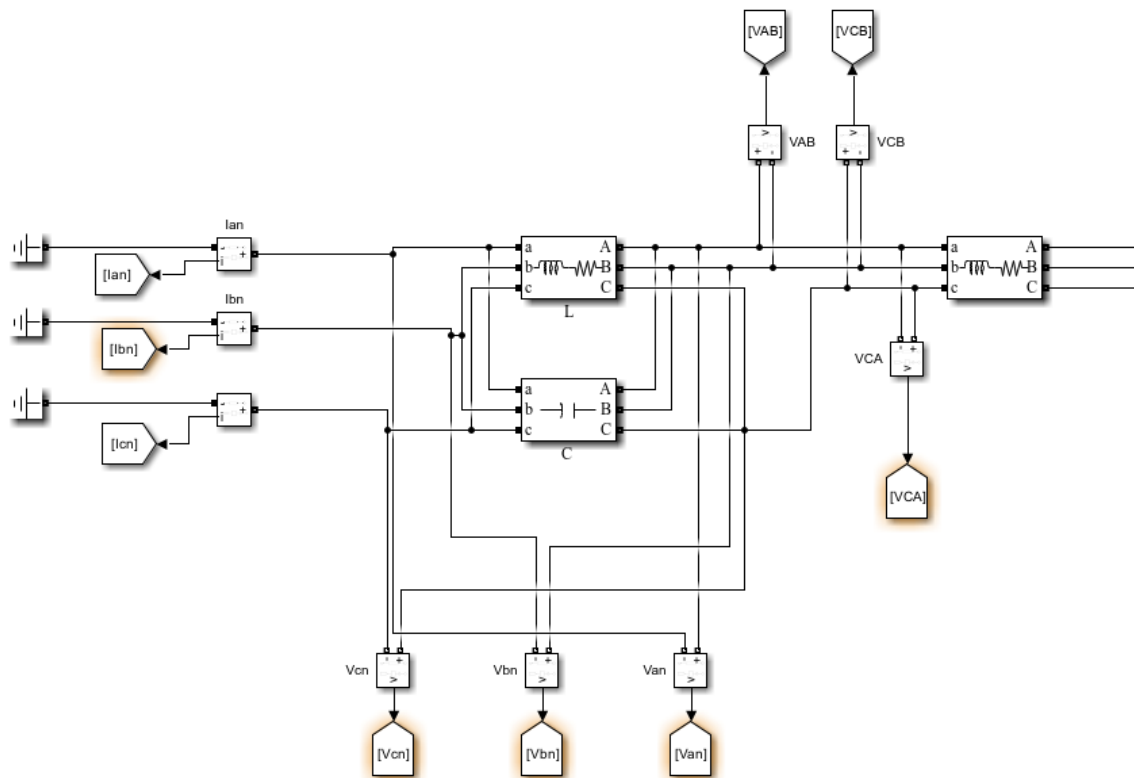
Now let's go ahead and confirm the accuracy of our calculations for the capacitor capacitance by measuring the power using the two-wattmeter method and show that the reactive power is zero!



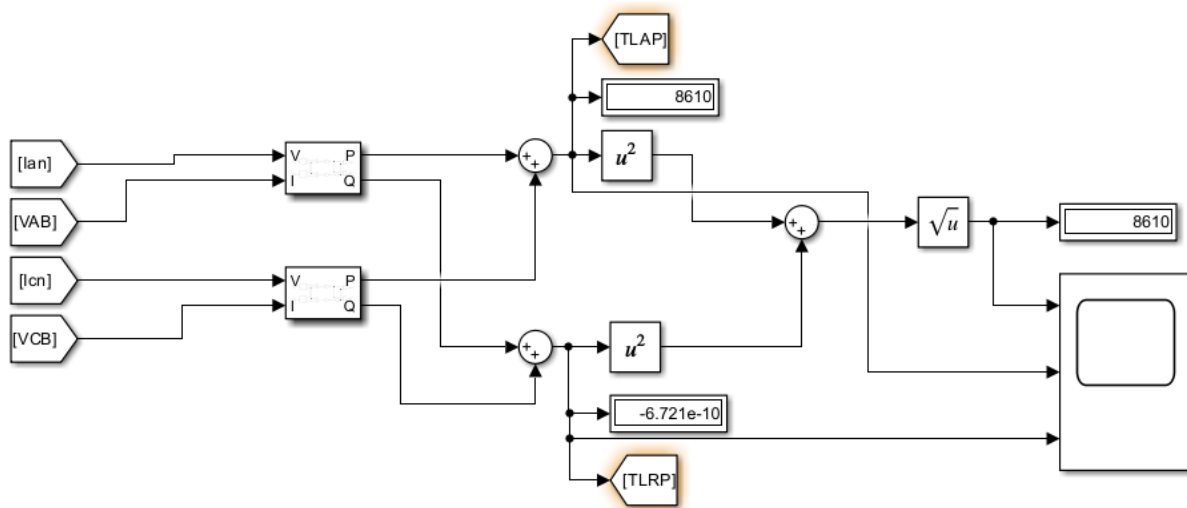

As we can see, the active power is 8610 watts and the reactive power is almost 0.


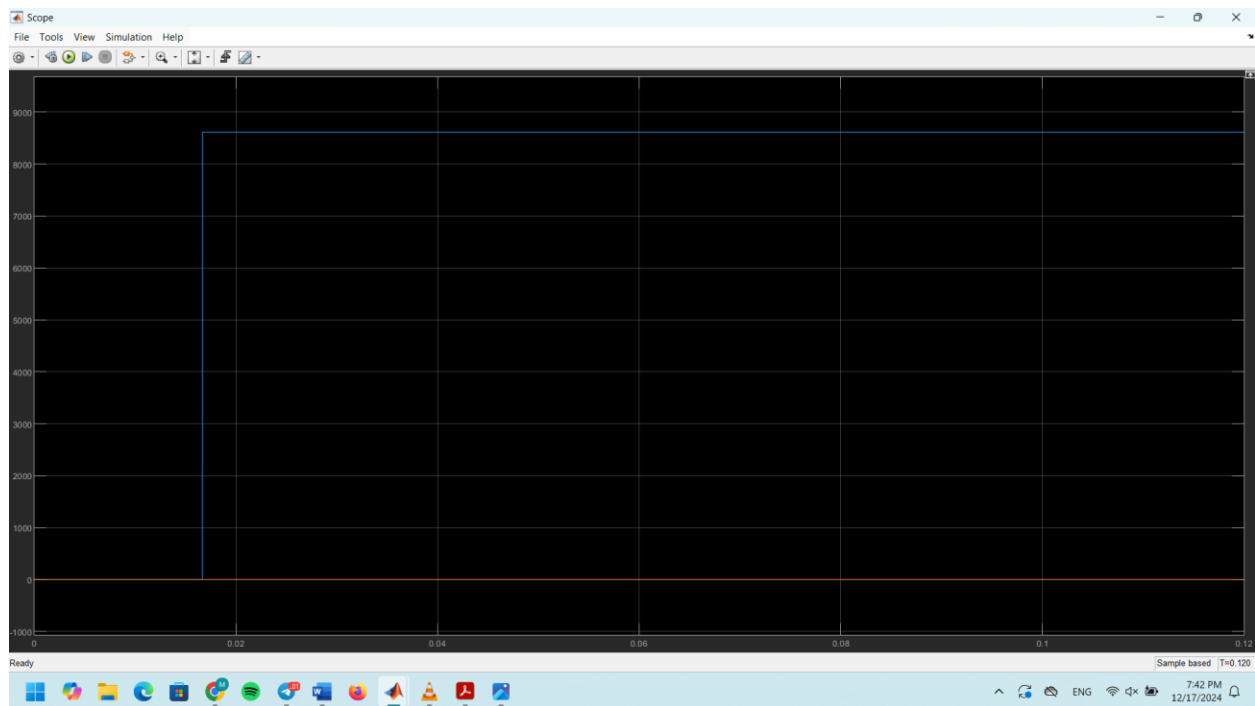
We see the active and reactive power diagram in the figure below:



Let's move on to the next question!

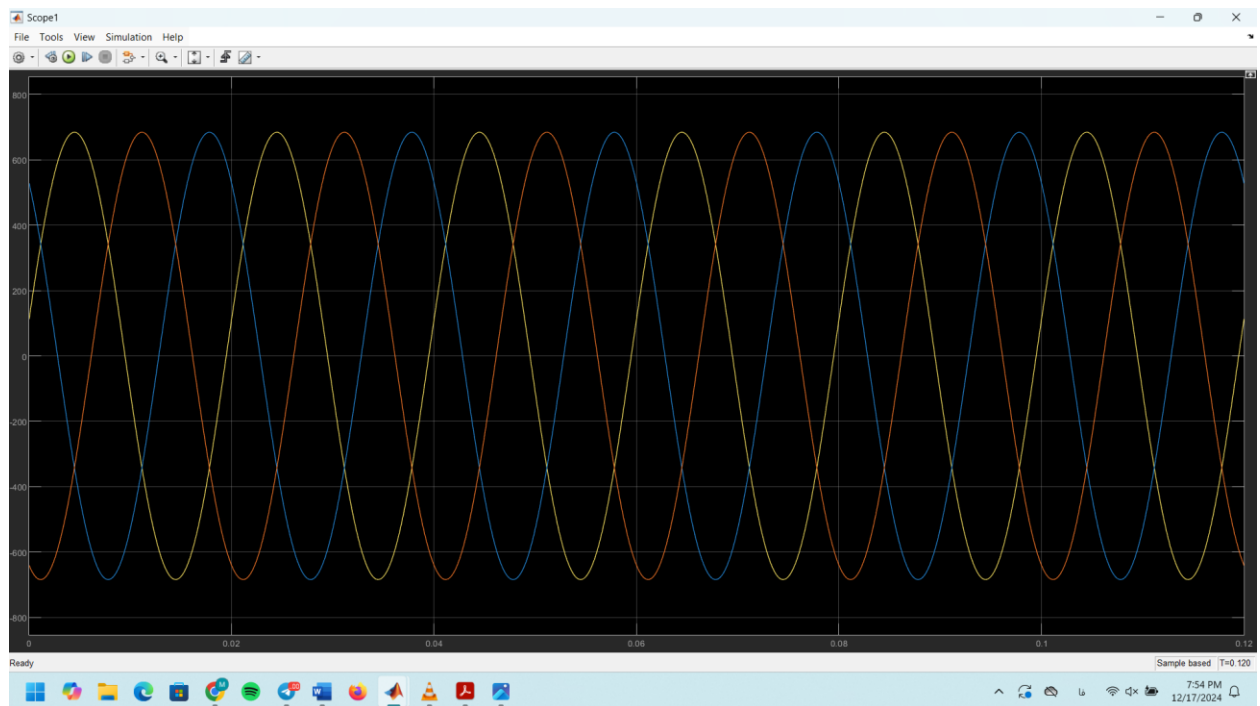
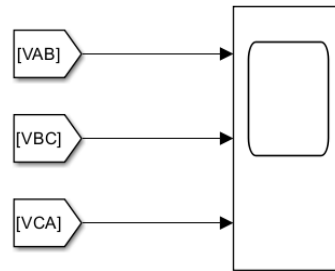
Q2)

We show the line voltage on the load side:




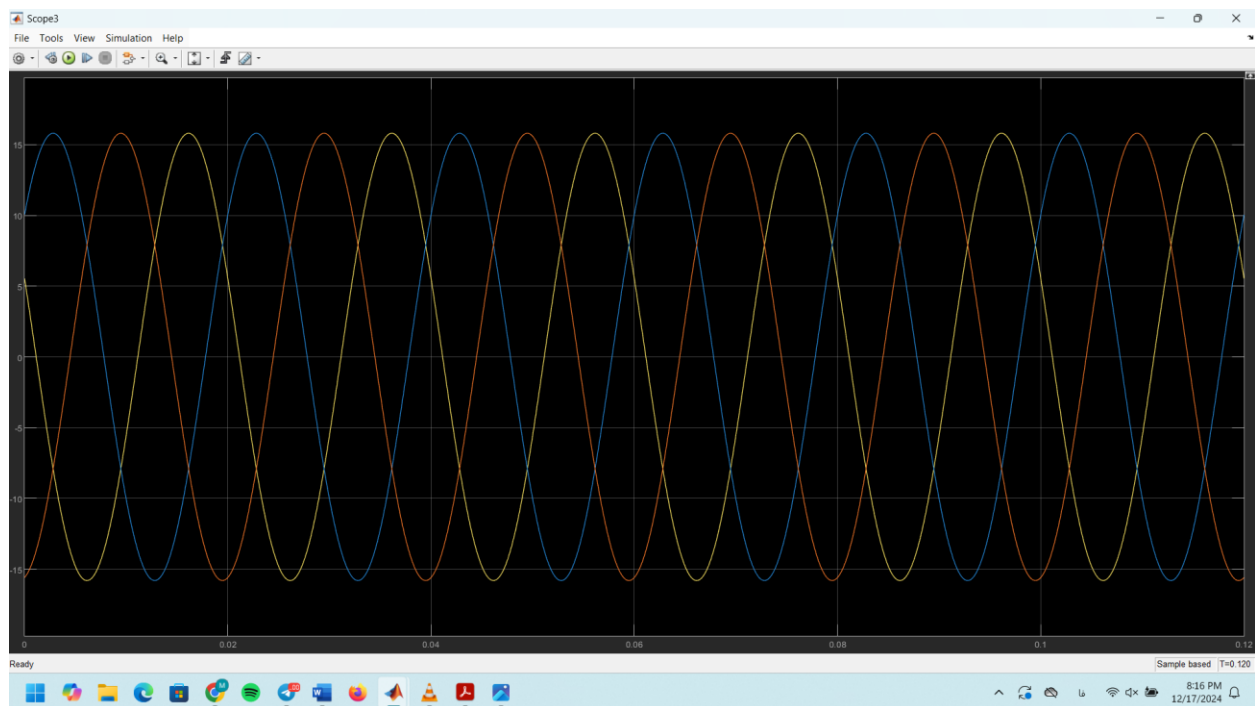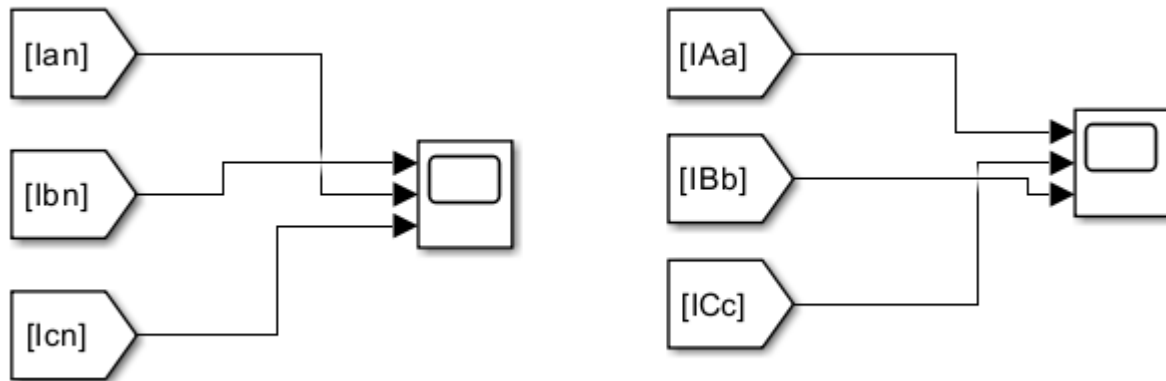Q3)

Now we want to show the line and phase current waveforms on the secondary side:



Phase current waveform

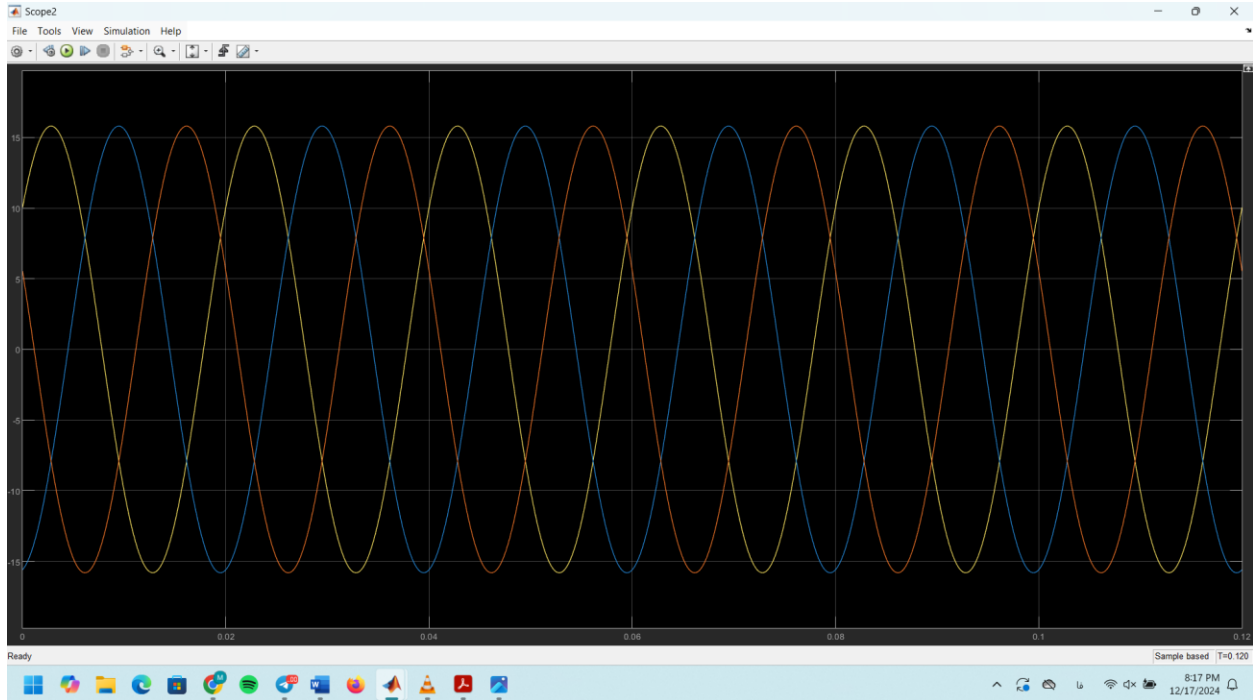




Line current waveform

It is clear that since our load is in a star shape, the line and phase currents are equal.


Q)4

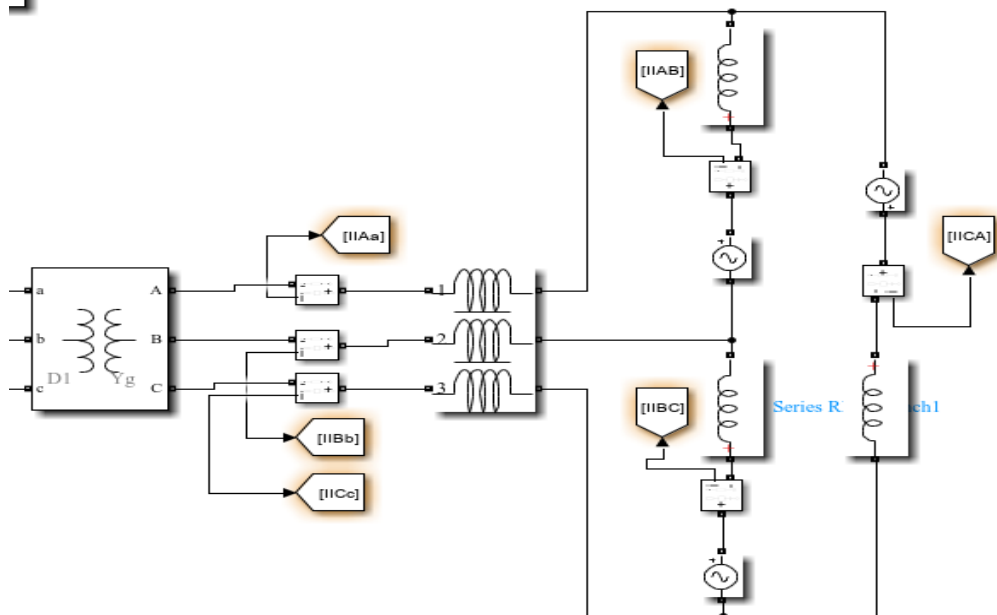Now we want to show the line and phase current waveforms on the source side:



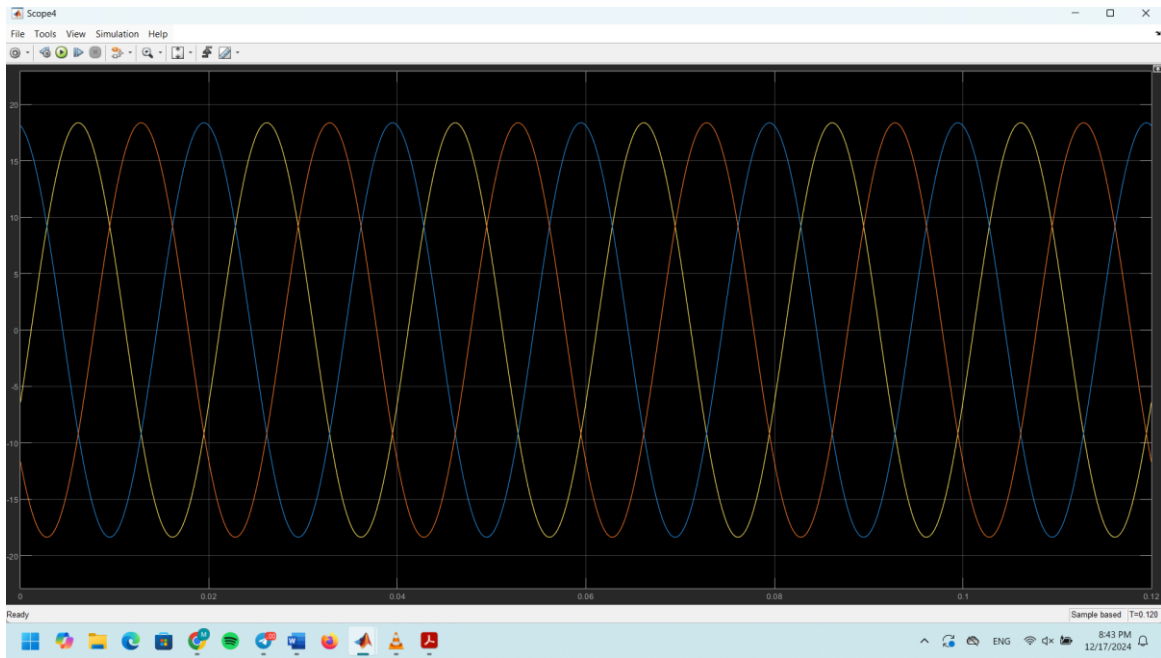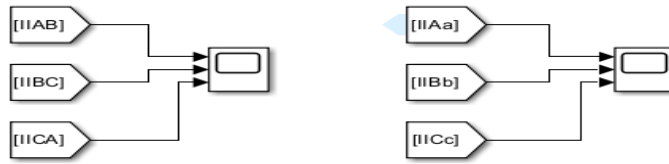


Phase current waveform

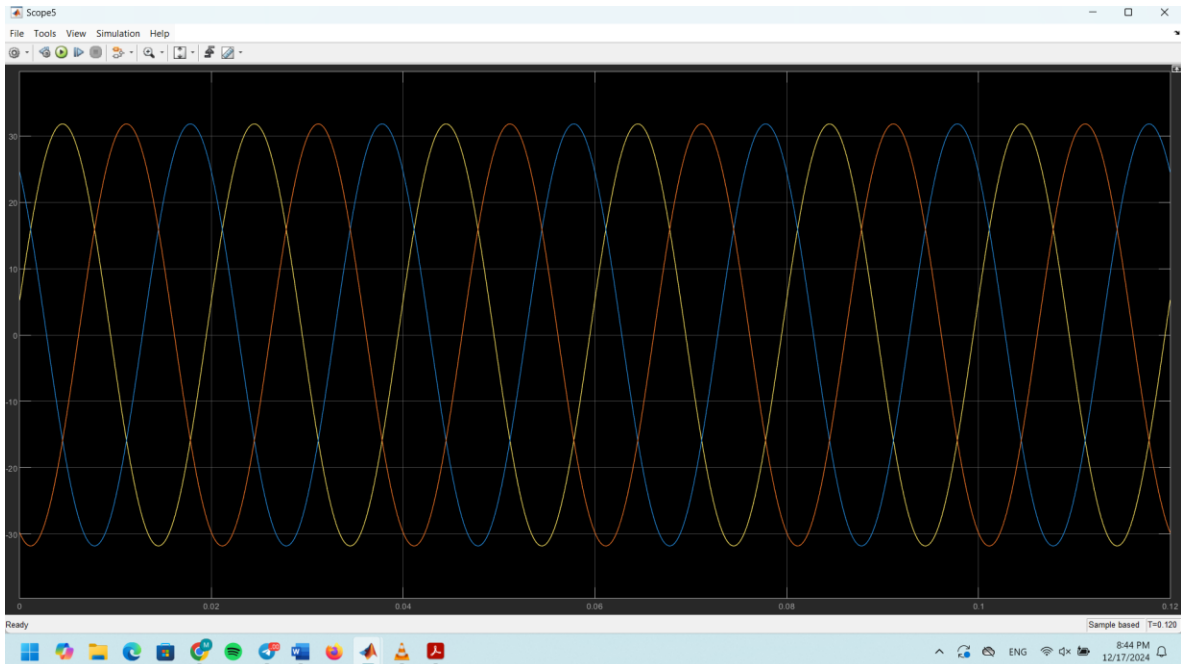


Line current waveform

On the source side, since the arrangement is in the form of a triangle, the current flowing through each voltage source is the line current, and the phase current is the current flowing through the transmission lines. Given their waveforms, the radical line current is 3 times the phase current, and its phase is 30 degrees ahead.

Q5)

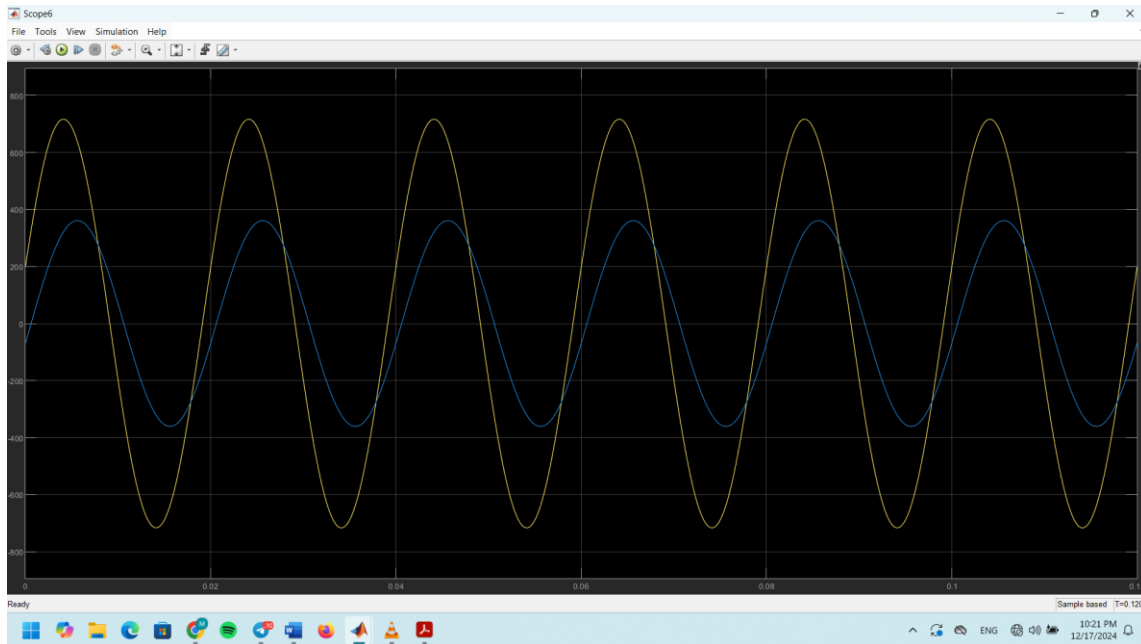

Primary and secondary side voltage

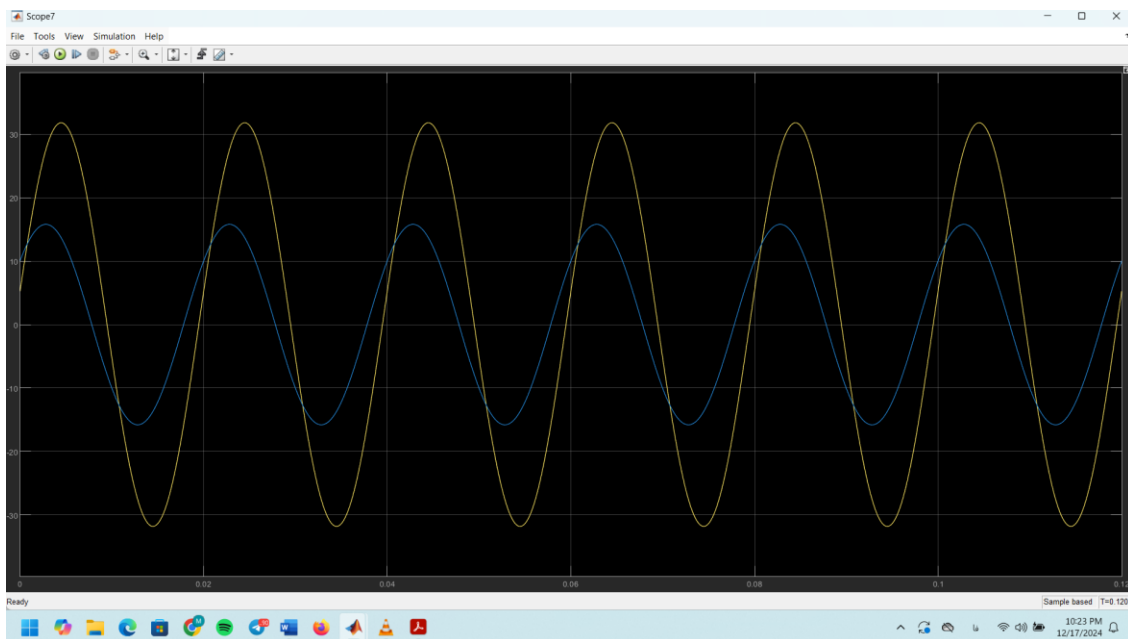


Primary and secondary side current



$$\left| \frac{V_2}{V_1} \right| = \frac{N_2}{N_1}$$

$$\left| \frac{I_2}{I_1} \right| = \frac{N_1}{N_2}$$

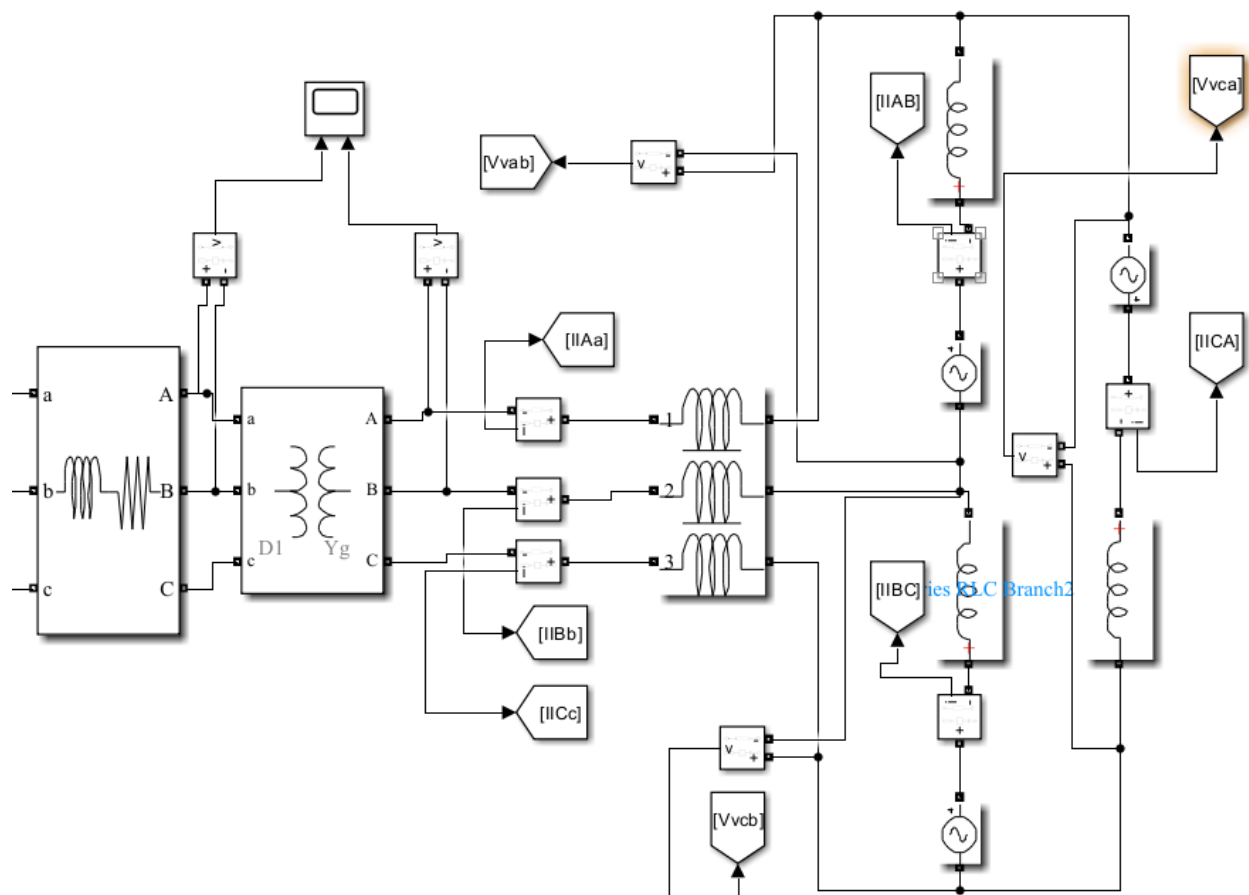Q6)


We use the same two-wattmeter method explained in the previous sections:



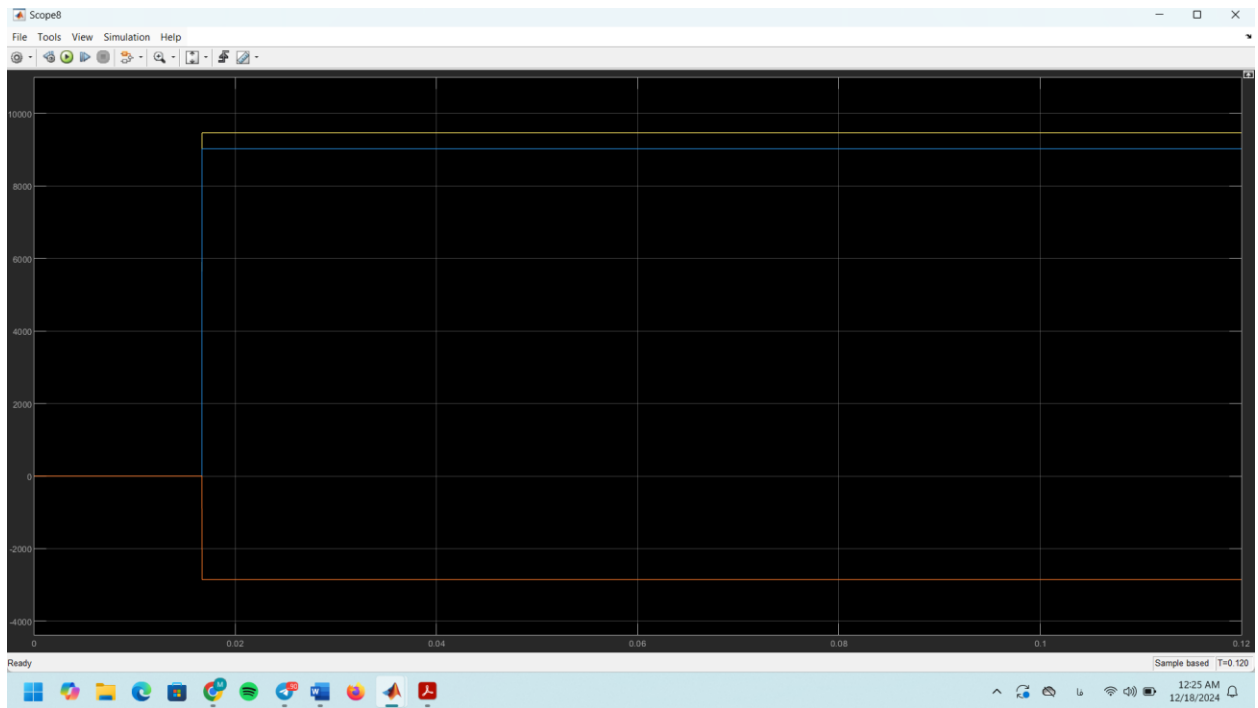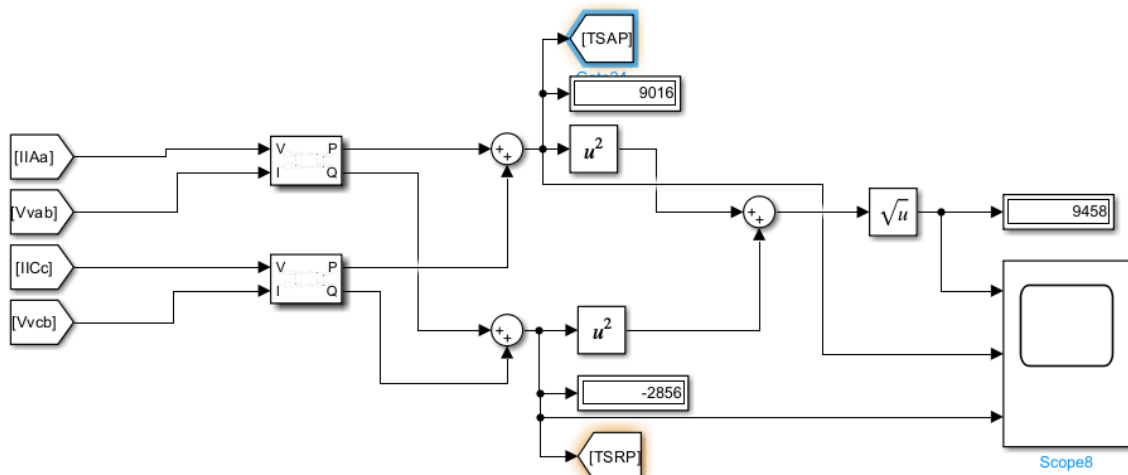

Apparent power waveform, active power and reactive power

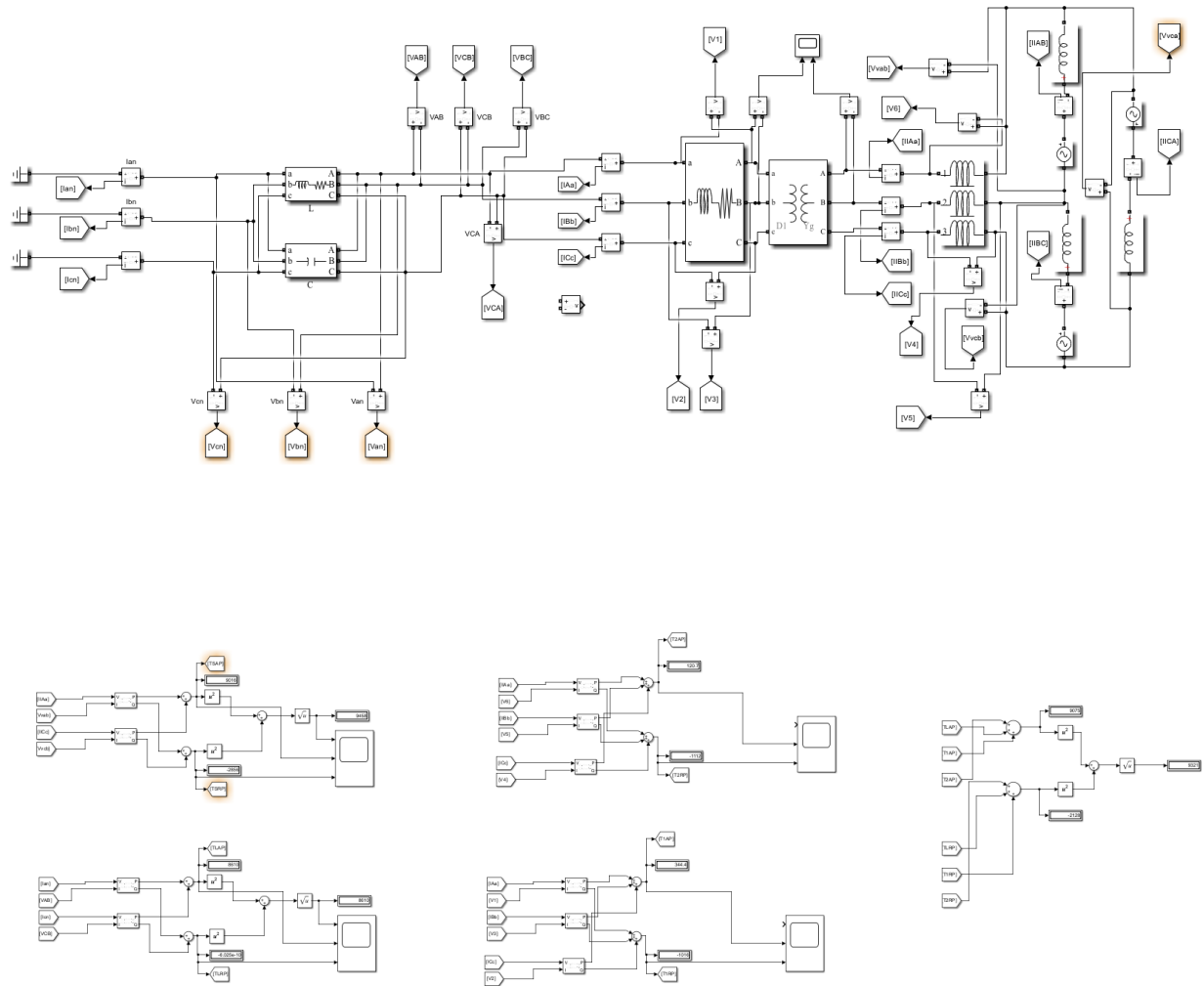Now we examine the power conservation theorem in the system:




The apparent power produced by the source is 9458 watts.

The apparent power consumed by the passive elements is 9321 watts, which is a good approximation of the power conservation equation.


The reason for this slight difference is that the elements are not ideal.

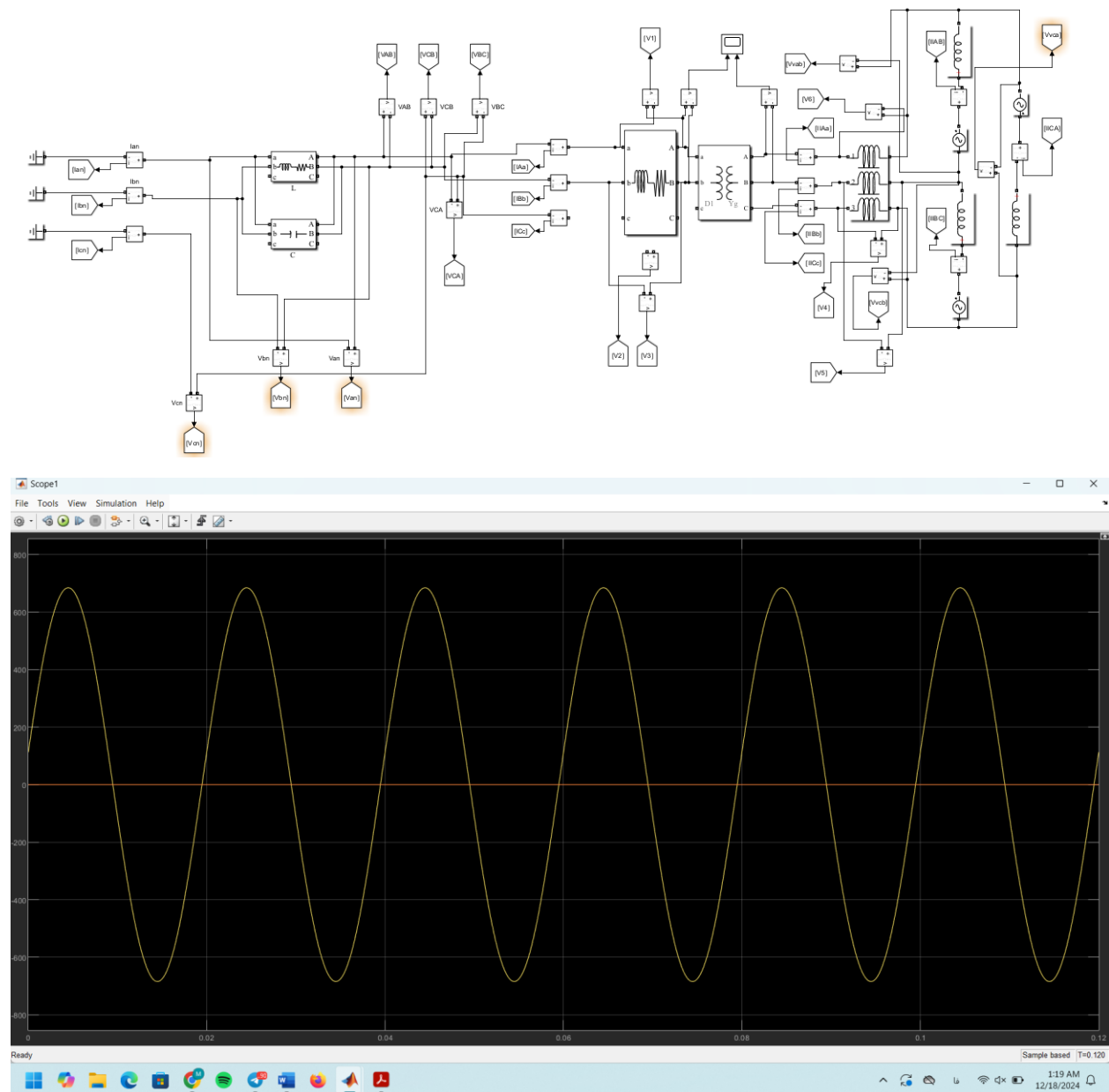Q7)


One of the transmission lines has been removed from the circuit:




Line voltages at both ends of the load

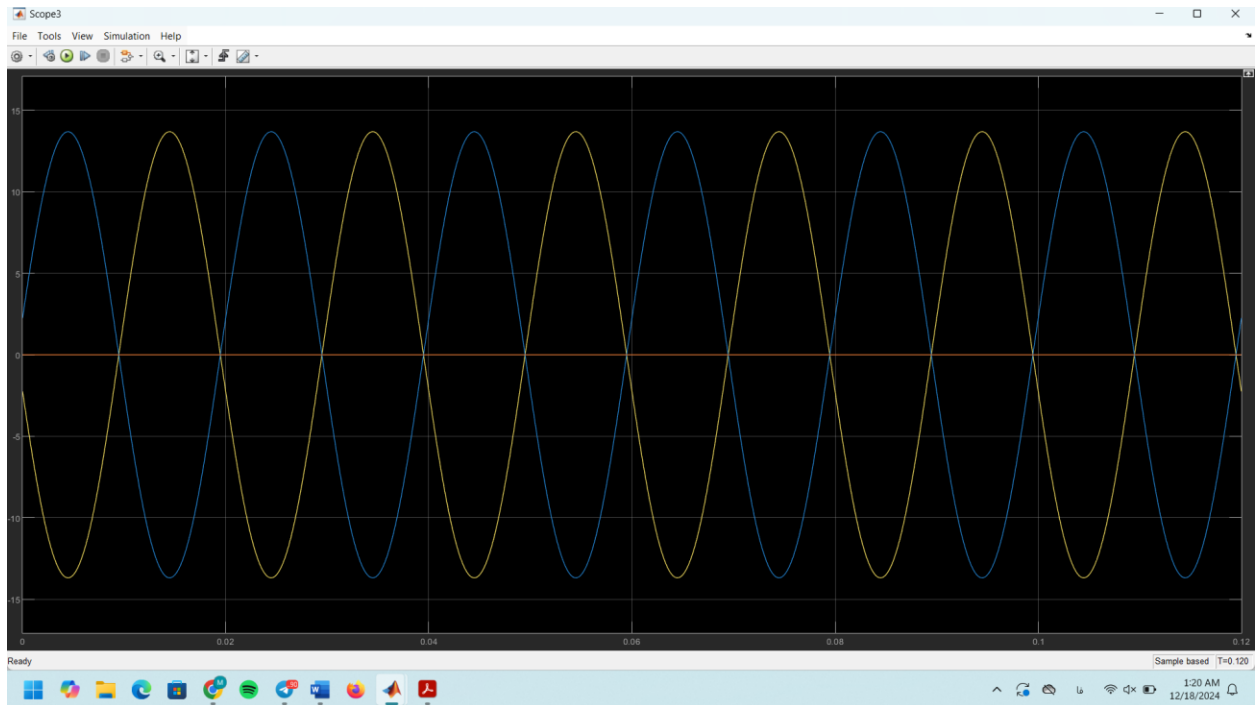


Phase current of loads

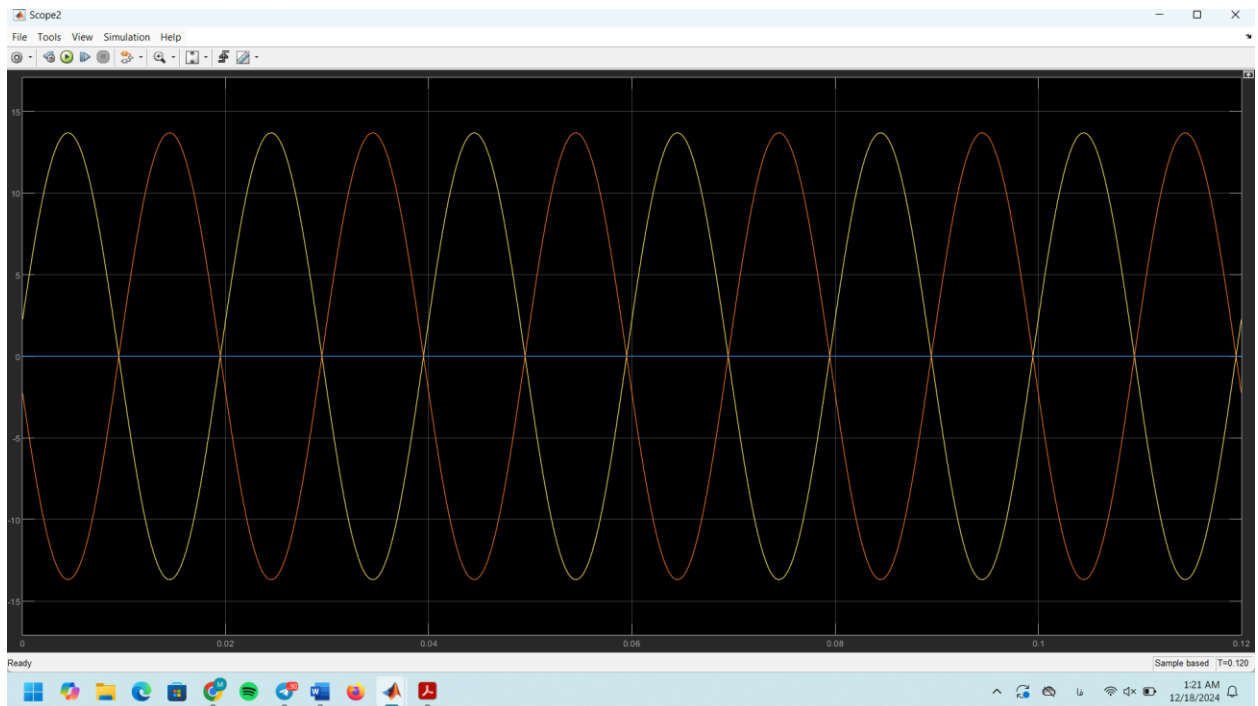


Load current of loads

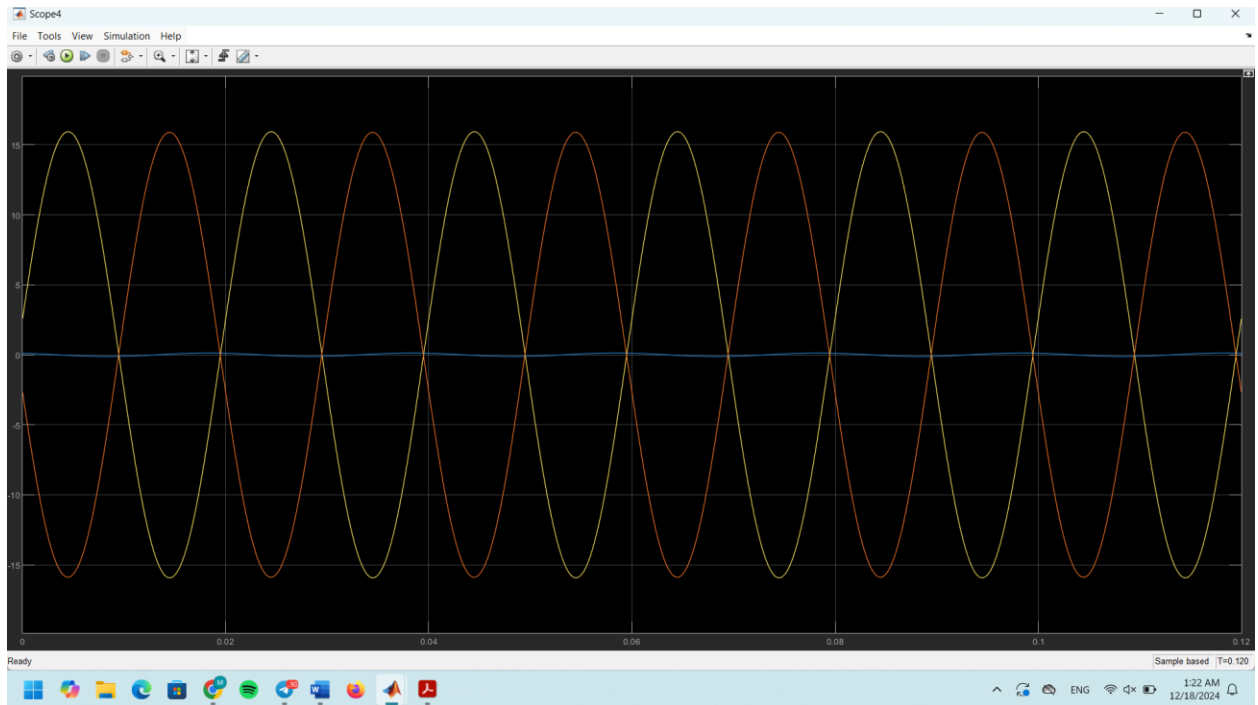

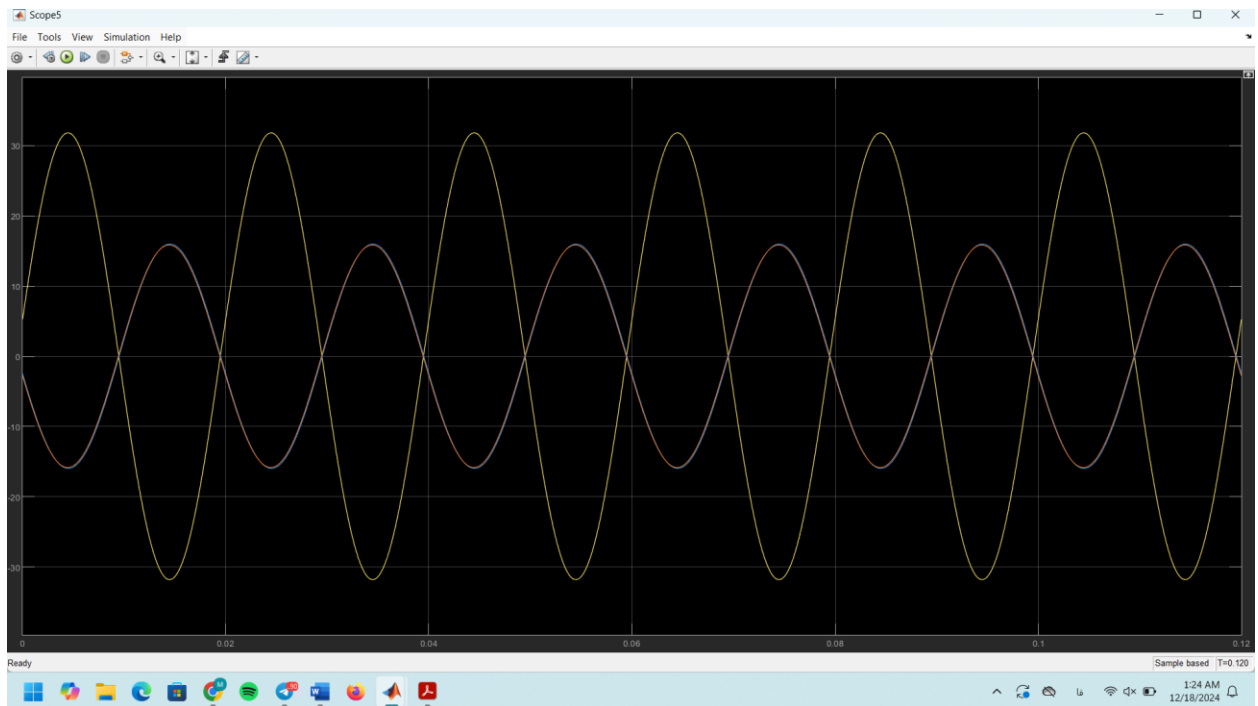Transmission line current on the primary side



Line current on the source side

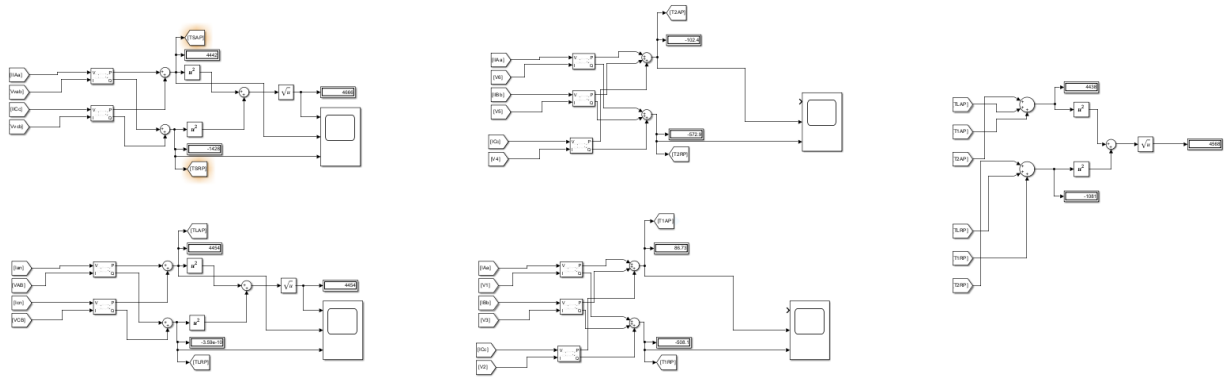

As we can see, the conservation of energy theorem also holds

As we can see, even though one of the secondary side windings is out of the circuit, the transformer is still capable of transmitting three-phase power to the load.

Q)8

The efficiency in a symmetrical three-phase system is 98.55 percent.

$$(9321/9458) \cdot 100 = 98.55$$

The efficiency in an asymmetric three-phase system is 97.89 percent.

$$(4568/4666) \cdot 100 = 97.89$$

As we can see, the efficiency has decreased.

